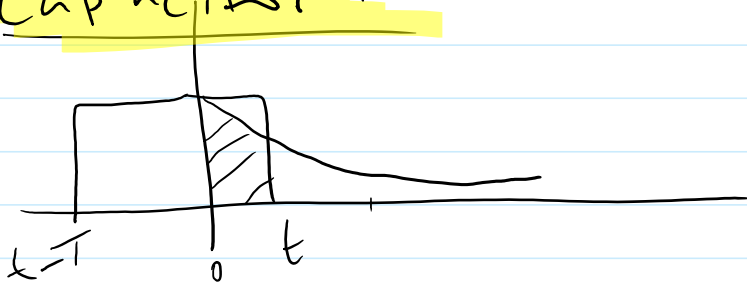


# PROJECT 2-GRADE SHEET

**Submission Page** Summary-Provide this page at the front of your project submission


Problem	Max Score	Score
Derivation	10	
2-A1	15	
2-A2	15	
2-B1	20	
2-B2	20	
2-B3	20	
<b>Total</b>	100	
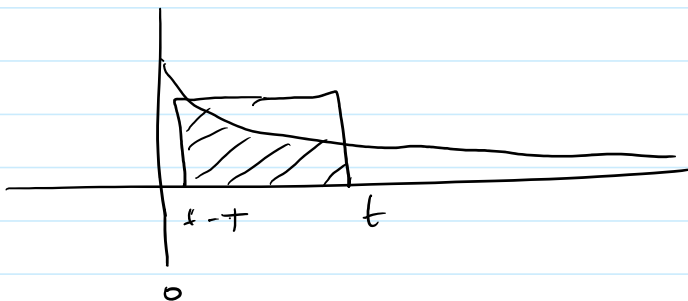
# CAPACITOR



$$t \geq 0, \\ t - T < 0 \Rightarrow \underline{0 \leq t < T}$$

$$\frac{A}{RC} \int_0^t e^{-T/RC} dT = -A \left[ e^{-T/RC} \right]_0^t \\ = A \left( 1 - e^{-t/RC} \right)$$



$$t - T \geq 0 \rightarrow \underline{t \geq T}$$

$$\frac{A}{RC} \int_{t-T}^t e^{-\tau/RC} d\tau = -A \left[ e^{-\tau/RC} \right]_{t-T}^t = A \left[ -e^{-t/RC} + e^{-(t-T)/RC} \right]$$

$$= A \left( e^{T/RC} - 1 \right) e^{-t/RC}$$

Resistor:

$$0 \leq t < T$$

$$\int_0^t \left[ f(\tau) - \frac{1}{RC} e^{-\tau/RC} \right] d\tau$$

$$= A \left[ u(\tau) + e^{-\tau/RC} \right]_0^t$$

$$= A \left[ u(t) + e^{-t/RC} - u(0) - 1 \right]$$

$$= A \begin{bmatrix} 1 + e^{-t/RC} & 0 & 1 \end{bmatrix}$$

$$= A e^{-t/RC}$$

$$\underline{t \geq T}$$

$$= \int_{t-T}^t \left( \delta(\tau) - \frac{1}{RC} e^{-\tau/RC} \right) d\tau$$

$$= A \left[ u(t) + e^{-t/RC} \right]_{t-T}^t$$

$$= A \left[ u(t) + e^{-t/RC} - u(t-T) + e^{-(t-T)/RC} \right]$$

$$= A \begin{bmatrix} e^{-t/RC} & (-t'/RC) \\ e & -e \end{bmatrix}$$

$$= A \left( 1 - e^{-t/RC} \right) e^{-t/RC}$$

---

```
close all; clear; clc
```

## PART A1

```
R = [600, 1000, 1200];
A = 5;
C = 1e-6;
T = 0.010;
T_end = 0.020;
t = 0:0.000001:0.020;

type('rc_voltages.m')

for m = 1:length(R)
    figure
    [V_c, V_r] = rc_voltages(R(m), C, A, T, T_end);
    plot(t, V_c(t), 'Linewidth', 2)
    hold on
    plot(t, V_r(t), 'Linewidth', 2)
    hold on
    plot(t, V_c(t) + V_r(t), '--c', 'Linewidth', 2)
    xlabel('time (s)')
    ylabel('voltage (V)')
    legend('V_c', 'V_r', 'impulse response')
    title([num2str(R(m)), ' ohms'])
    grid on
end
```

## PART A2

```
R = 1000;
A = 5;
C = 1e-6;
T = 0.010;
T_end = 0.020;
t = 0:0.000001:0.060;
delay = [0.007 0.012 0.017];
for i = 1:length(delay)
    figure,
    [V_c, V_r] = rc_voltages(R, C, A, T, T_end);
    plot(t, V_c(t) + V_c(t-delay(i)) + V_c(t-2*delay(i)), 'Linewidth',
    2);
    hold on
    plot(t, V_r(t) + V_r(t-delay(i)) + V_r(t-2*delay(i)), 'Linewidth',
    2)
    hold on
    plot(t, V_c(t) + V_r(t) + V_c(t-delay(i)) + V_r(t-delay(i)) +
    V_c(t-2*delay(i)) + V_r(t-2*delay(i)), '--c', 'Linewidth', 2)
    xlabel('time (s)')
    ylabel('voltage (V)')
    legend('V_c', 'V_r', 'impulse response')
```

---

```
        title([num2str(delay(i)*1000), ' ms'])  
        grid on  
    end
```

*Published with MATLAB® R2017a*

---

## Table of Contents

.....	1
B1 .....	1
B2 .....	2
B3 .....	3

```
close all, clear all, clc
```

## B1

```
R = 1000;
C = 0.000001;


% matlab
t = 0:0.000001:0.020;
x1 = (1/(R*C))*exp(-t/(R*C)).*(t>=0);
x2 = heaviside(t) + -1 * heaviside(t-0.01);
y = (conv(x1,x2)) * 0.000001;
y = 1 - y(1:20001);
y(10000:20001) = y(10000:20001) - 1;
plot(t, y, 'Linewidth', 2)
hold on

% simulated
data = xlsread('multisim_data_r.xlsx');
t = data(:,1);
y = data(:,2);
plot(t, y, '--r', 'Linewidth', 2)

% measured
t = 0:0.00002:0.020;
data = xlsread('mydaq_data_r.xlsx');
plot(t, data, ':g', 'Linewidth', 2)

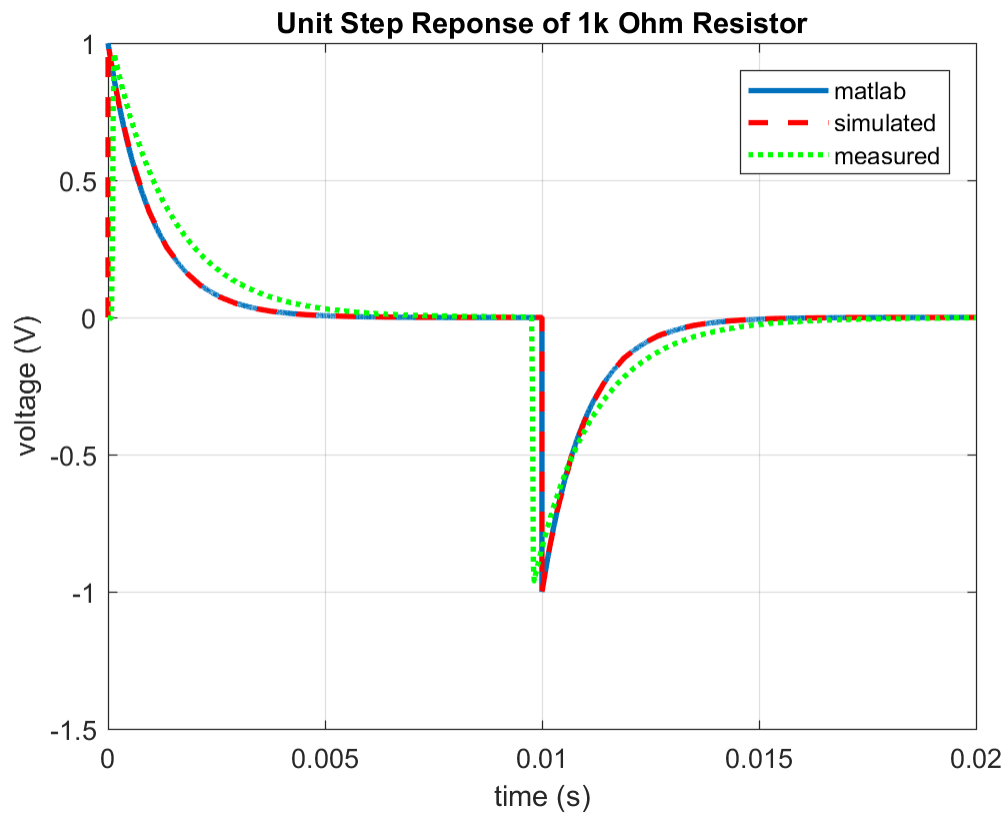title('Unit Step Reponse of 1k Ohm Resistor')
xlabel('time (s)')
ylabel('voltage (V)')
legend('matlab', 'simulated', 'measured')
grid on
```





## B2

```
R = 1000;
C = 0.000001;
A = 1;

figure
% ideal capacitor voltage
T = 0.010;
T_end = 0.020;
[V_c, ~] = rc_voltages(R, C, A, T, T_end);
plot(t, V_c(t), 'Linewidth', 2)
hold on

% discrete convolution
t = 0:0.000001:0.020;
x1 = (1/(R*C))*exp(-t/(R*C)).*(t>=0);
x2 = heaviside(t) + -1 * heaviside(t-0.01);
y = (conv(x1,x2)) * 0.000001;
plot(t, y(1:20001), '--y', 'Linewidth', 2);
hold on

% simulated
data = xlsread('multisim_data_c.xlsx');
t = data(:,1);
```

---


```

y = data(:,2);
plot(t, y, '--r', 'Linewidth' , 2)

% measured
t = 0:0.00002:0.020;
data = xlsread('mydaq_data_c.xlsx');
plot(t, data, ':g', 'Linewidth', 2)

title('Unit Step Reponse of 1 uF Capacitor')
xlabel('time (s)')
ylabel('voltage (V)')
legend('ideal', 'matlab', 'simulated', 'measured')
grid on

```

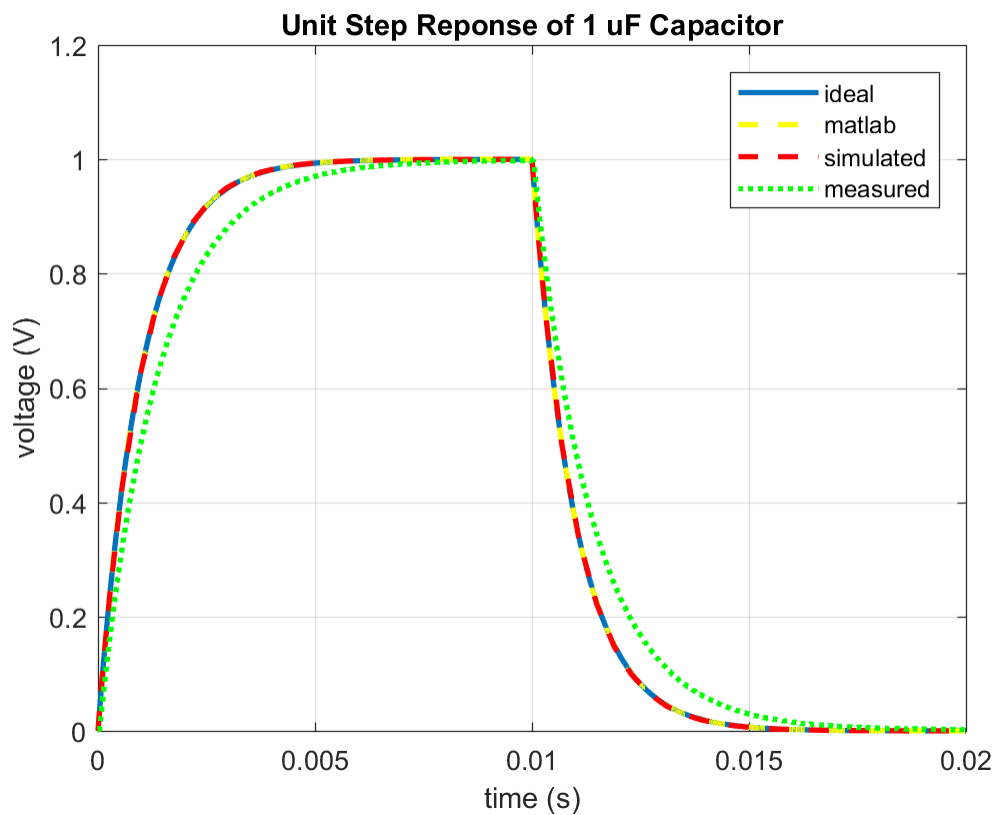

## B3

```

figure
% measured
t = 0:0.00002:0.020;
data = xlsread('mydaq_data_c.xlsx');
plot(t,data, 'Linewidth' , 2)
hold on

% fitted
t_o = 0.01;

```

---

```

V_o = 1;
V_c = @(tau, t) (t < t_o & t >= 0) .* (V_o .* (1 - exp(-t/(tau)))) ...
    + (t >= t_o) .* (V_o .* (1 - exp(-t_o/(tau))) .* exp(-(t - t_o)/
    (tau)));
yi=data(end);
idx=max(find(abs(y - yi) >= 0.37 * yi));
tau_est = data(idx);
tau_est = lsqcurvefit(V_c, tau_est, t', data);
plot(t, V_c(tau_est, t), '--', 'Linewidth', 2)
hold on

title('Unit Step Reponse of 1 uF Capacitor')
xlabel('time (s)')
ylabel('voltage (V)')
ylim([0 1.2])
legend('measured', 'fitted')
grid on

figure
% ideal impulse response
syms T t
f = @(T, t) (V_o .* (1 - exp(-t/(T))));
H_c = matlabFunction(diff(f(T, t)));

tau = R*C;
t = 0:0.000001:0.020;
plot(t, H_c(tau, t), 'Linewidth', 2)
hold on

% estimated impulse response
syms T t
f = @(T, t) (V_o .* (1 - exp(-t/(T))));
H_c = matlabFunction(diff(f(T, t)));



t = 0:0.000001:0.020;
plot(t, H_c(tau_est, t), '--', 'Linewidth', 2)

title('Impulse Reponse of 1 uF Capacitor')
xlabel('time (s)')
ylabel('voltage rate of change (V/s)')
legend('ideal', 'estimated')
grid on

```

*Local minimum possible.*

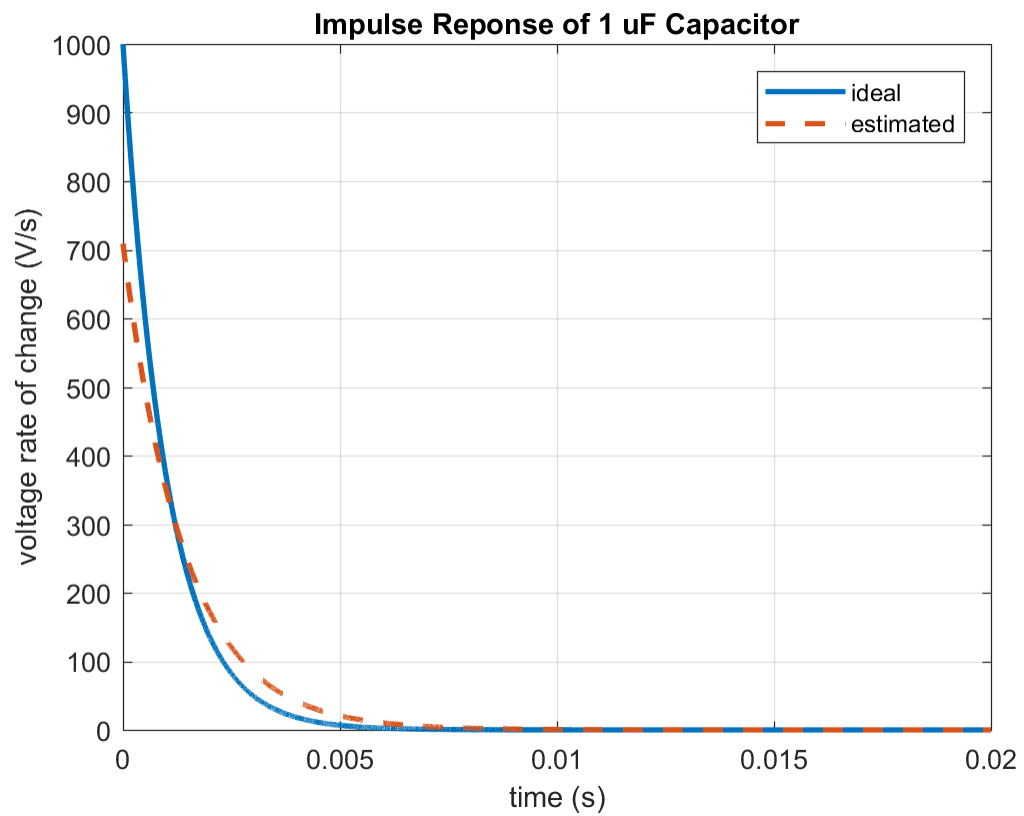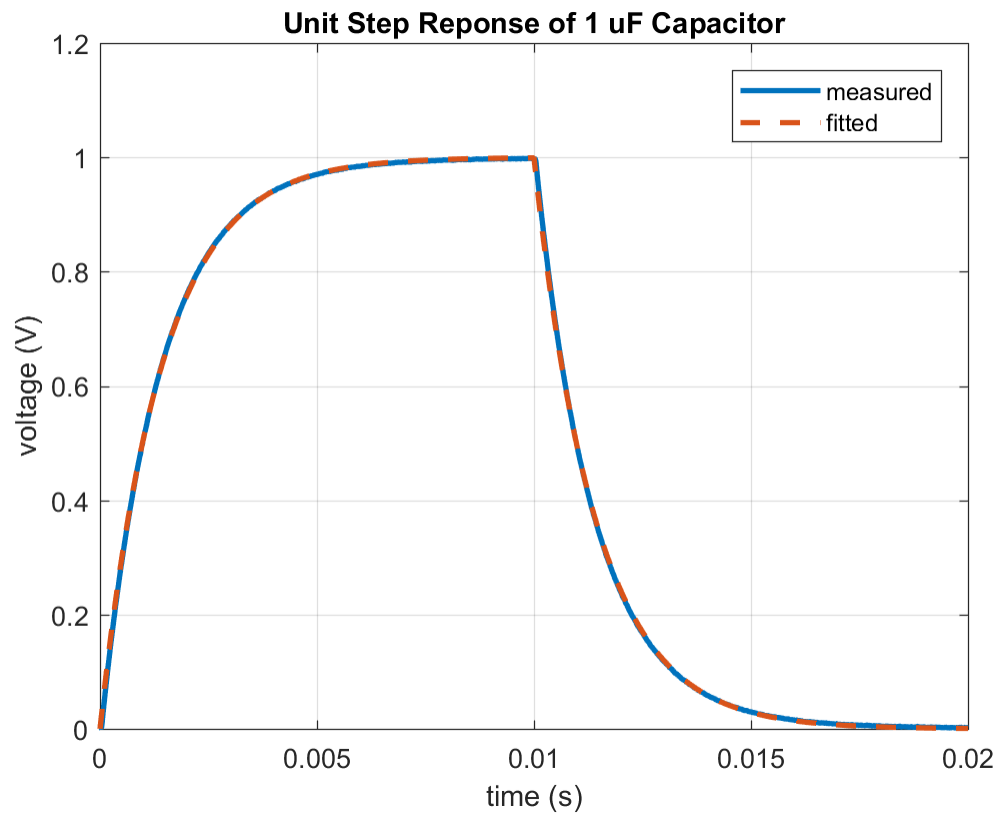*lsqcurvefit stopped because the final change in the sum of squares relative to its initial value is less than the default value of the function tolerance.*



---

*Published with MATLAB® R2017a*